

Lecture 32, Dec 1, 2022

Timing Analysis

- So far we've assumed that our gates operate with zero delay, but this is not true
- Capacitance of wires and gates introduce delay, which determines the clock speed
- Consider:

```
module muxDFF(input logic w, r, L, E, clock,
              output logic Q);
    always_ff @(posedge clock)
        if (L)
            Q <= r;
        else if (E)
            Q <= w;
endmodule

module shift4(input logic [3:0] SW, KEY,
              output logic [3:0] LEDR);
    logic [3:0] Q;
    muxDFF u3(KEY[0], SW[3], KEY[2], KEY[1], KEY[3], Q[3]);
    muxDFF u2(Q[3], SW[2], KEY[2], KEY[1], KEY[3], Q[2]);
    muxDFF u1(Q[2], SW[1], KEY[2], KEY[1], KEY[3], Q[1]);
    muxDFF u0(Q[1], SW[0], KEY[2], KEY[1], KEY[3], Q[0]);
    assign LEDR = Q;
endmodule
```

- What is the maximum clock frequency at which this circuit can operate?
 - t_{CQ} is the “clock to Q” propagation delay, time delay from clock change to output observed
 - There are also delays through the muxes before we're ready to load D again
- Timing analysis for the flip flops:
 - *Setup time* (t_{su}): D has to have been stable for some amount of time before the clock edge
 - *Hold time* (t_h): D has to be held stable for some amount of time after the clock edge
- The minimum clock period $T_{min} = t_{CQ} + t_{mux} + t_{mux} + t_{su}$
 - The signal must propagate through the first flip flop and then two muxes, and then be stable for some amount of time
 - $F_{max} = \frac{1}{T_{min}}$
- When doing the analysis we look at flip-flop to flip-flop paths, from a source to a sink, and we find the longest path

Clock Skew

- It is possible for the clock edge to not arrive at the same time to all the flip flops
 - On a large chip there can be significant delay in the wires
- On a diagram this is shown as a box with a delta in it, to show the possibility of skew
- We measure the skew time as $t_{skew} = \text{arrival time of clock at the sink} - \text{arrival time of clock at the source}$
 - The sink takes its input from the output of the source
- Skew can be positive or negative
 - Positive skew allows us to operate at a higher frequency, since this gives more time between the rising edge of the source clock to the next rising edge of the sink clock
 - Negative skew gives a lower maximum frequency
 - The effective period is reduced/elongated by the skew time

Set-Up Time Violation

- Find all paths between flip flops, and look for the longest such path, including setup time
- Another way to think about the setup-time violation is that the logic is too slow for the data to arrive at the input of the sink before the clock changes
- The constraint is $t_{min} \geq t_{CQ} + t_{logic,max} + t_{su} + \Delta$